

---

# PROJECT IITB\_RISC\_PIPELINE

---

E KRITHEESH (200070018)

AKSHAY VERMA (200070005)


ANKITH R (200070006)

GOWTHAM S (20D070031)


---

## Level 2 Flowcharts


ADD & NDU:

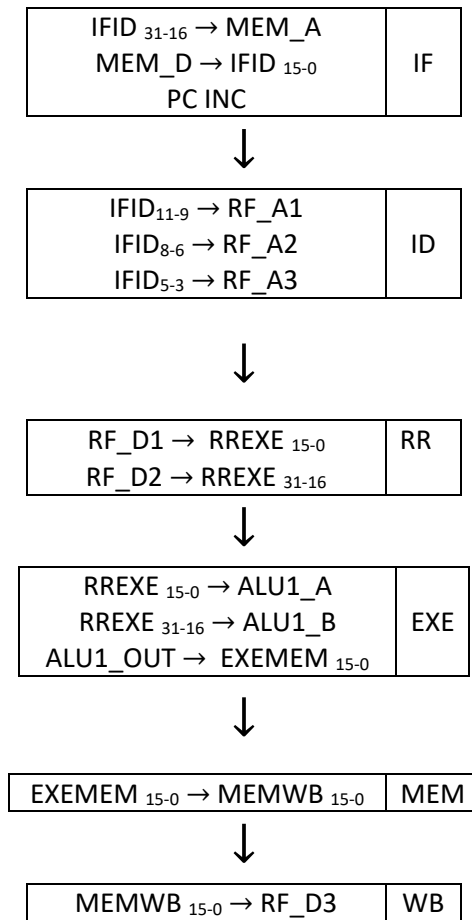


ADC/ADZ/NDC/NDZ:

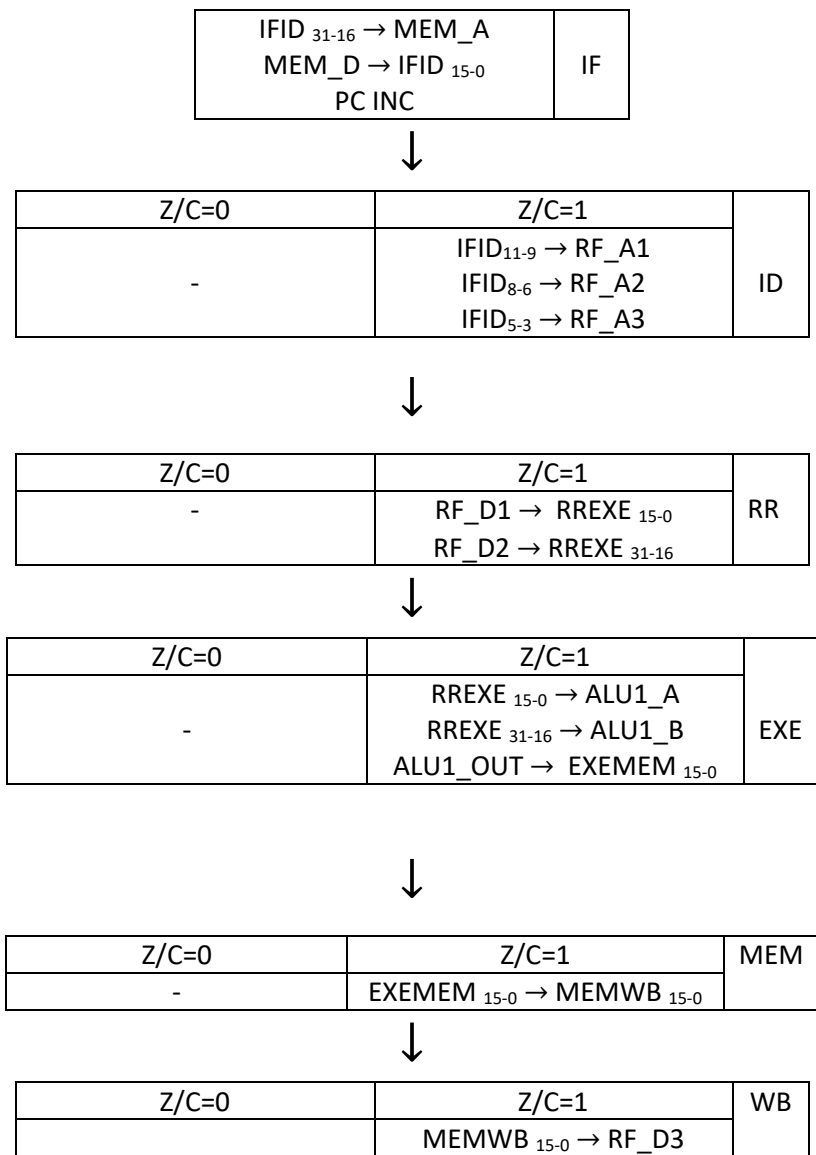


ADL:

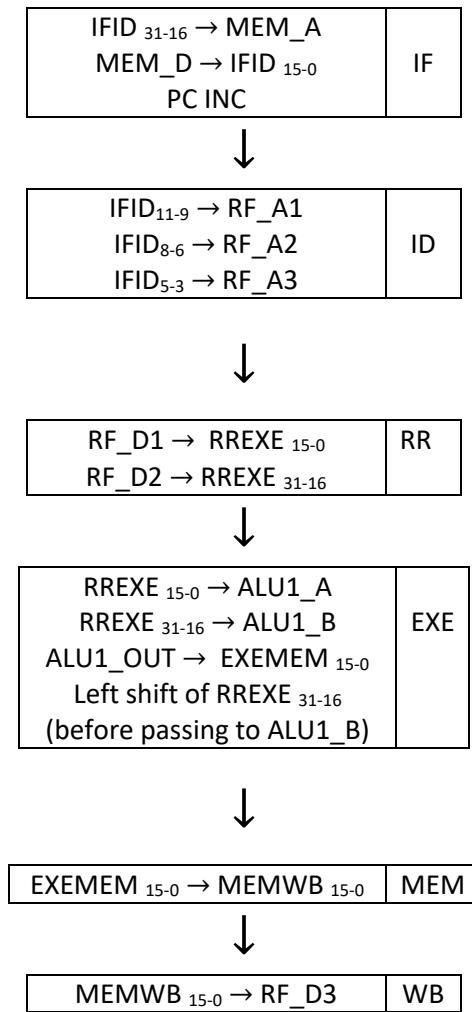


ADI:

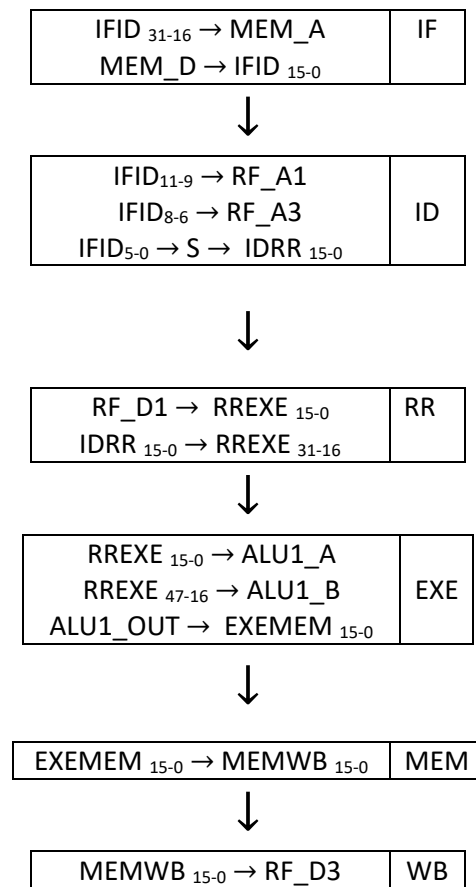


LHI:

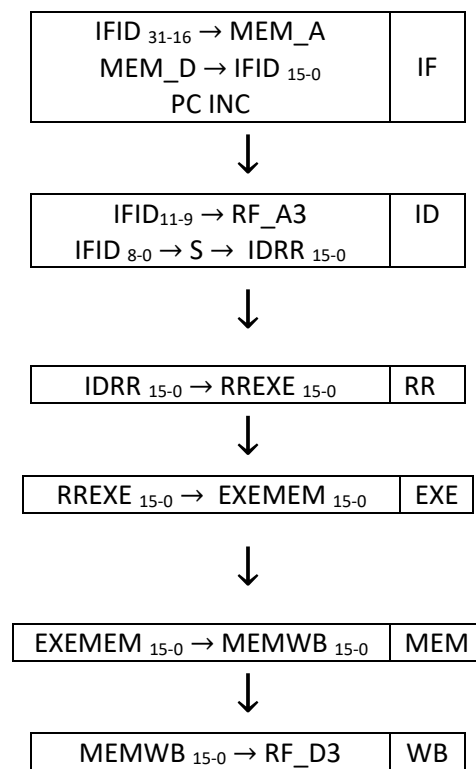


LW:

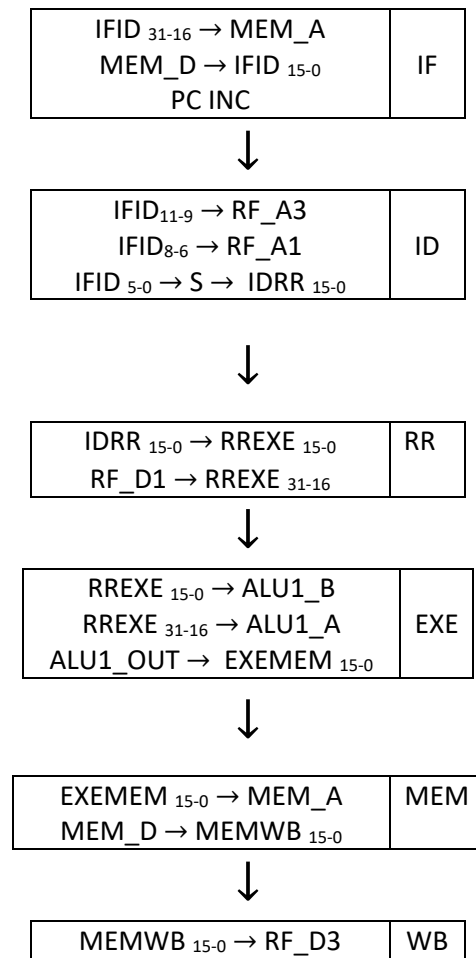


SW:

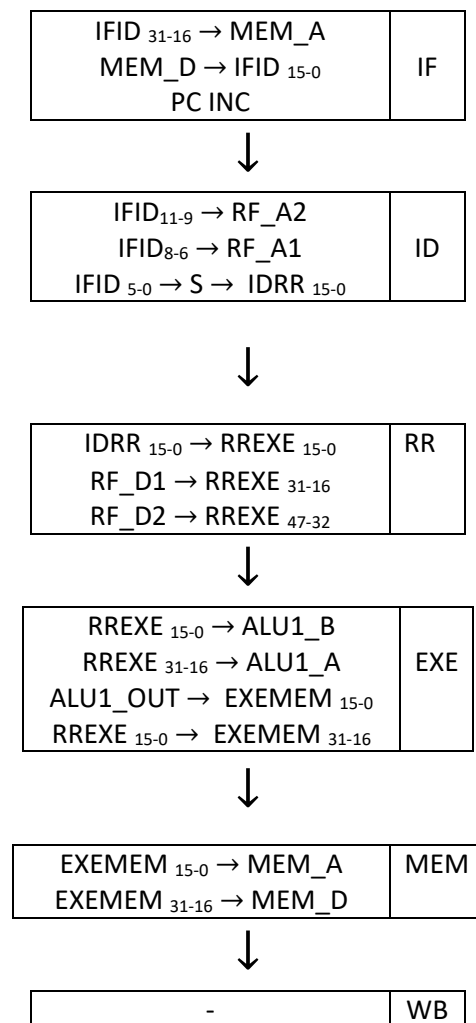


JRI:

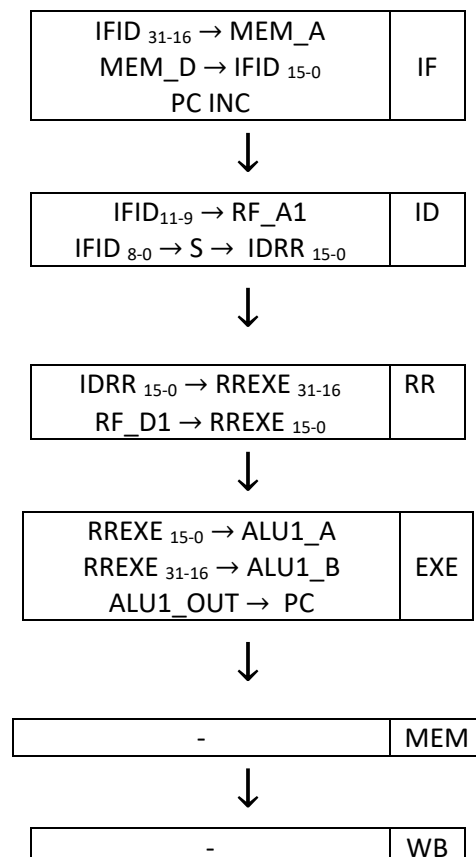


JLR:

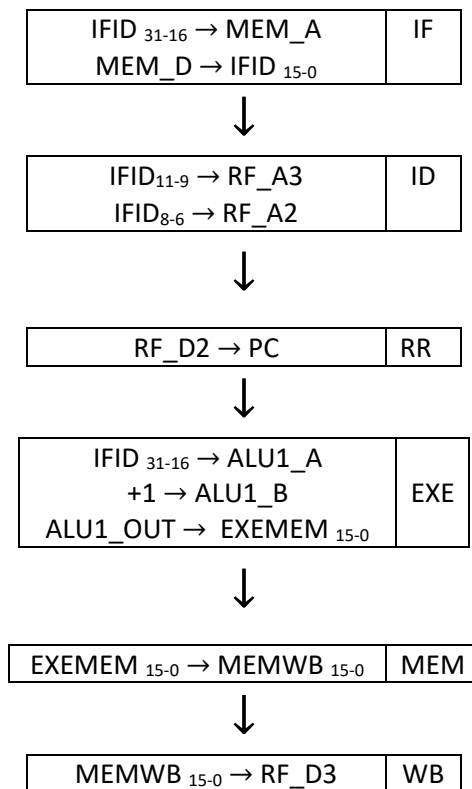

JAL:

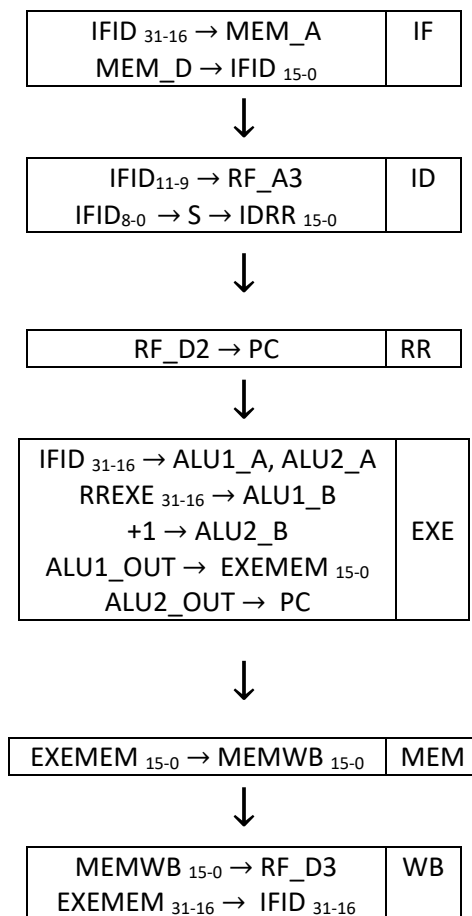


BEQ:

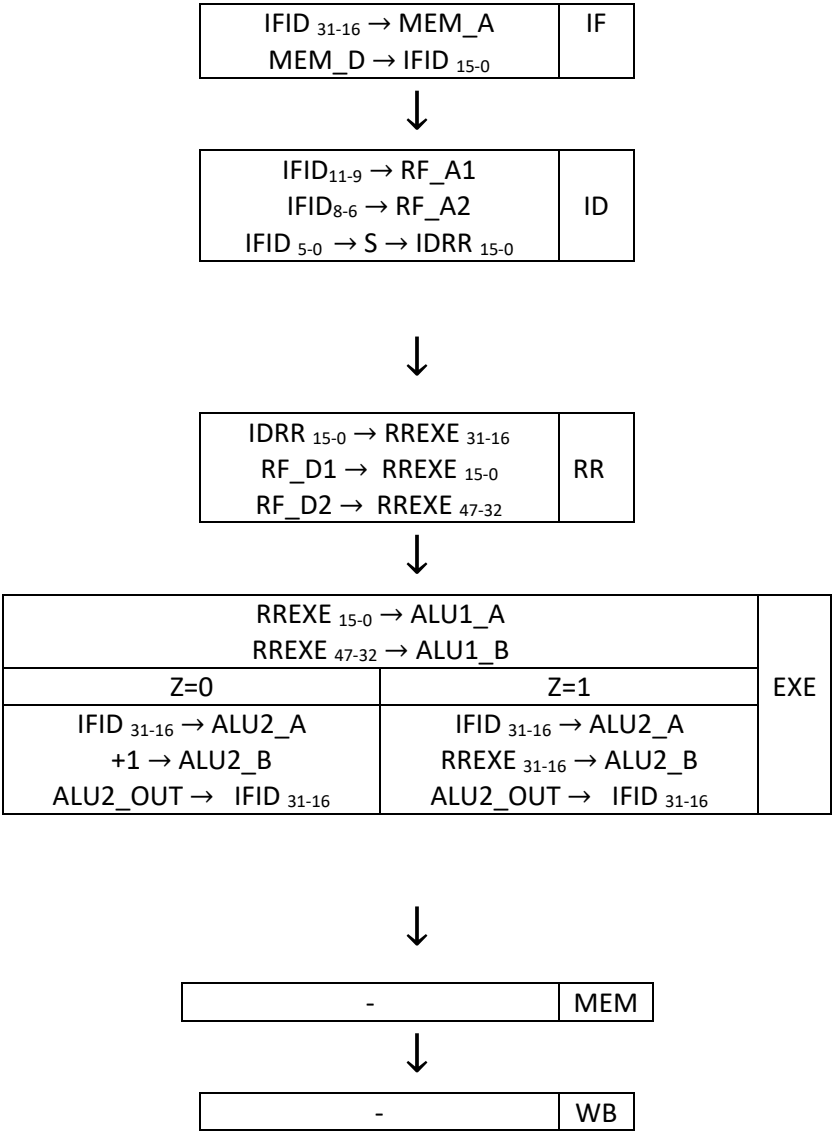




# DATAPATH

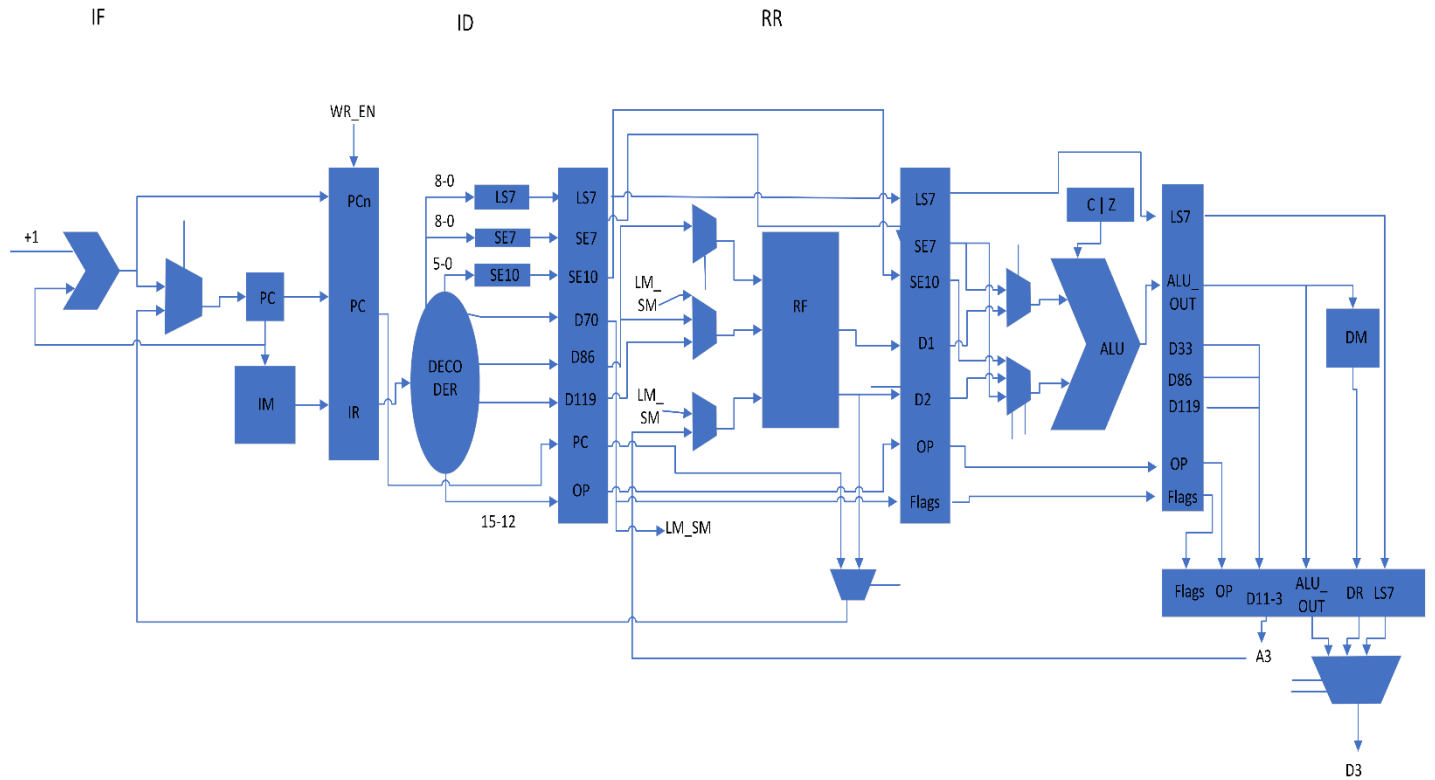

# FORWARDING UNIT


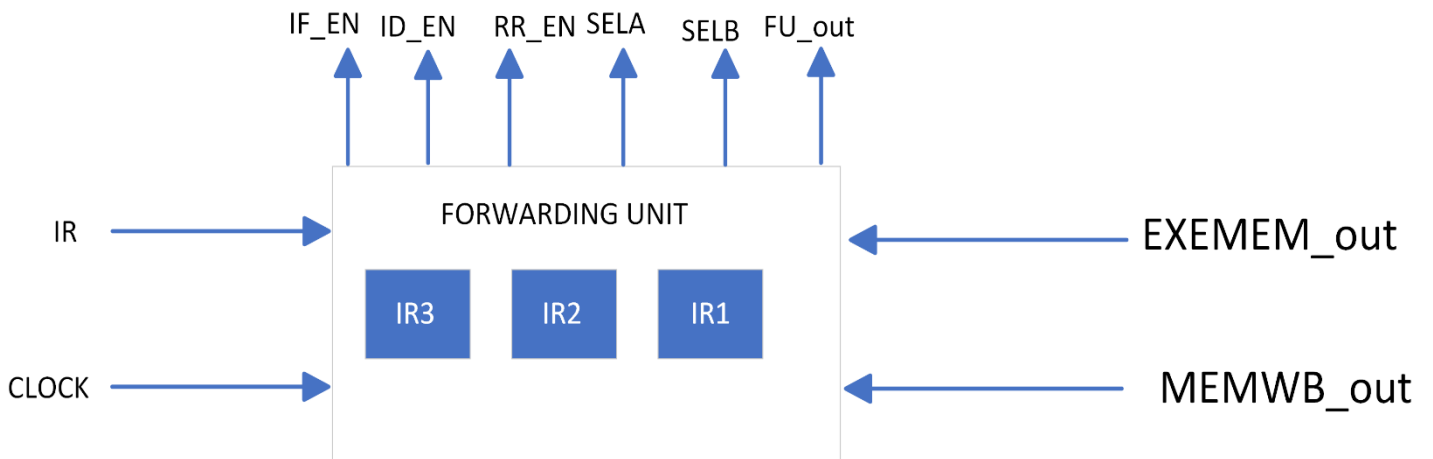


## FORWARDING UNIT TABLE

Current Instruction(I1)	Next or Next to Next Instruction(I2)	Forwarding
ADD/ADC (with C=1)/ ADZ (with Z=1)/ NDU/NDC/ NDZ/ADL	ADD/ADC/ADZ/ADL/ ADI/NDU/NDC/NDZ/ BEQ/SW	if $IR_{5-3}^1 = IR_{11-9}^2$ or $IR_{8-6}^2$ then ALU_A(or ALU_B) = EXE_MEM_ALU_out  if $IR_{5-3}^1 = IR_{11-9}^3$ or $IR_{8-6}^3$ then ALU_A(or ALU_B) = MEM_WB_ALU_out
ADD/ADC (with C=1)/ ADZ (with Z=1)/ NDU/NDC/ NDZ/ADL	JRI/SM/LM/ADI	if $IR_{5-3}^1 == IR_{11-9}^2$ then ALU_A = EXE_MEM_ALU_out  if $IR_{5-3}^1 == IR_{11-9}^3$ then ALU_A = MEM_WB_ALU_out
ADD/ADC (with C=1)/ ADZ (with Z=1)/ NDU/NDC/ NDZ/ADL	LW/JLR	if $IR_{5-3}^1 == IR_{8-6}^2$ then ALU_B = EXE_MEM_ALU_out  if $IR_{5-3}^1 == IR_{8-6}^3$ then ALU_B = MEM_WB_ALU_out
ADI	ADD/ADC/ADZ/ADL/ ADI/NDU/NDC/NDZ/ BEQ/SW	if $IR_{8-6}^1 = IR_{11-9}^2$ or $IR_{8-6}^2$ then ALU_A(or ALU_B) = EXE_MEM_ALU_out  if $IR_{8-6}^1 = IR_{11-9}^3$ or $IR_{8-6}^3$ then ALU_A(or ALU_B) = MEM_WB_ALU_out
ADI	JRI/SM/LM/ADI	if $IR_{8-6}^1 == IR_{11-9}^2$ then ALU_A = EXE_MEM_ALU_out  if $IR_{8-6}^1 == IR_{11-9}^3$ then ALU_A = MEM_WB_ALU_out
ADI	LW/JLR	if $IR_{8-6}^1 == IR_{8-6}^2$ then ALU_B = EXE_MEM_ALU_out  if $IR_{8-6}^1 == IR_{8-6}^3$ then ALU_B = MEM_WB_ALU_out
JLR/LHI/JAL	ADD/ADC/ADZ/ADL/ ADI/NDU/NDC/NDZ/ BEQ/SW	if $IR_{11-9}^1 = IR_{11-9}^2$ or $IR_{8-6}^2$ then ALU_A(or ALU_B) = EXE_MEM_ALU_out  if $IR_{11-9}^1 = IR_{11-9}^3$ or $IR_{8-6}^3$ then ALU_A(or ALU_B) = MEM_WB_ALU_out
JLR/LHI/JAL	JRI/SM/LM/ADI	if $IR_{11-9}^1 == IR_{11-9}^2$ then ALU_A = EXE_MEM_ALU_out  if $IR_{11-9}^1 == IR_{11-9}^3$ then ALU_A = MEM_WB_ALU_out

JLR/LHI/JAL	LW/JLR	<p>if <math>IR_{11-9}^1 == IR_{8-6}^2</math> then ALU_B = EXE_MEM_ALU_out</p> <p>if <math>IR_{11-9}^1 == IR_{8-6}^3</math> then ALU_B = MEM_WB_ALU_out</p>
LW	ADD/ADC/ADZ/ADL/ ADI/NDU/NDC/NDZ/ BEQ/SW	<p>if <math>IR_{11-9}^1 == IR_{11-9}^2</math> or <math>IR_{8-6}^2</math> then 1) STOP FOR ONE CLOCK CYCLE 2) ALU_A (or ALU_B) = MEM_WB_ALU_out</p> <p>if <math>IR_{11-9}^1 == IR_{11-9}^3</math> or <math>IR_{8-6}^3</math> then ALU_A (or ALU_B) = MEM_WB_ALU_out</p>
LW	JRI/SM/LM/ADI	<p>if <math>IR_{11-9}^1 == IR_{11-9}^2</math> or <math>IR_{8-6}^2</math> then 1) STOP FOR ONE CLOCK CYCLE 2) ALU_A = MEM_WB_ALU_out</p> <p>if <math>IR_{11-9}^1 == IR_{11-9}^3</math> or <math>IR_{8-6}^3</math> then ALU_A = MEM_WB_ALU_out</p>
LW	LW/JLR	<p>if <math>IR_{11-9}^1 == IR_{8-6}^2</math> or <math>IR_{8-6}^2</math> then 1) STOP FOR ONE CLOCK CYCLE 2) ALU_B = MEM_WB_ALU_out</p> <p>if <math>IR_{11-9}^1 == IR_{8-6}^3</math> or <math>IR_{8-6}^3</math> then ALU_B = MEM_WB_ALU_out</p>

## BRANCH PREDICTOR

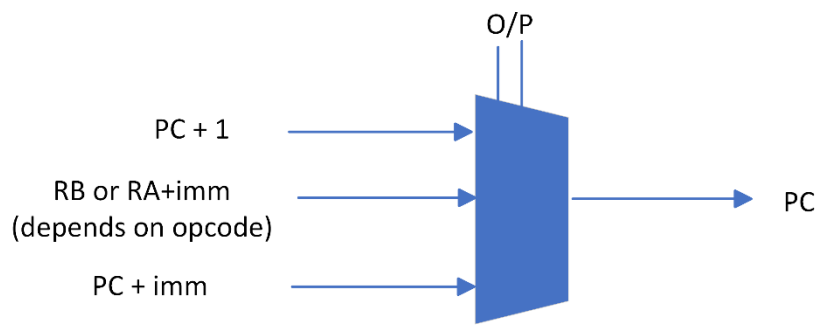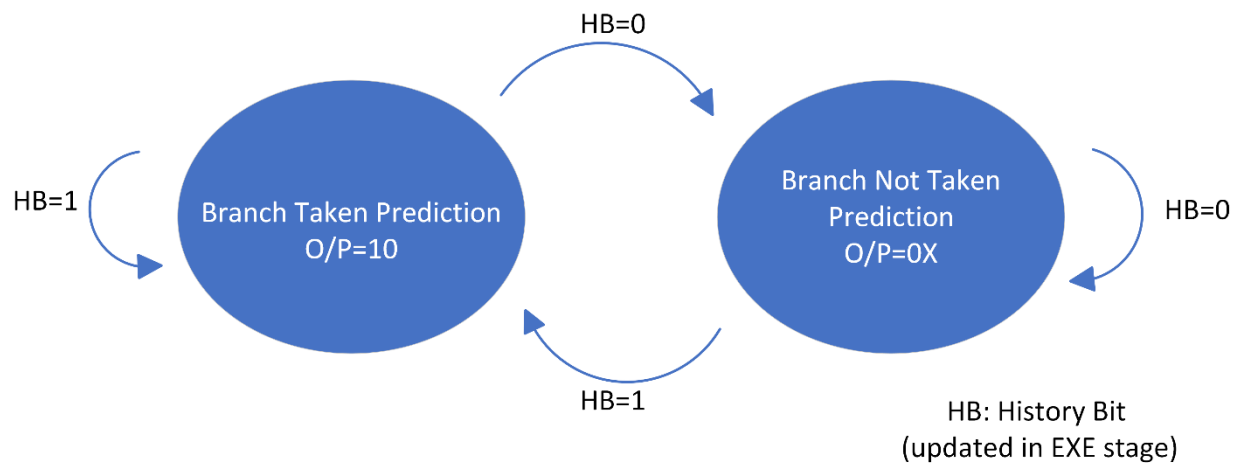

RTL View

